

CIRCUIT THEORY

1.3 Superposition Theorem | 1.4 Thevenin's Theorem | 1.5 Norton's Theorem | 1.6 Maximum Power Transfer Theorem | 1.7 Related Numerical Problems

Diploma / Polytechnic Engineering — Study Notes

1.3 Superposition Theorem

Definition

Statement: In any linear, bilateral network containing more than one independent source, the current through (or voltage across) any element is equal to the algebraic sum of the currents (or voltages) produced by each independent source acting alone, with all other independent sources replaced by their internal resistances (voltage sources short-circuited and current sources open-circuited).

Procedure / Steps

1. Select one independent source and replace all other voltage sources by a short circuit and all other current sources by an open circuit.
2. Redraw the simplified circuit and find the current/voltage in the desired branch using Ohm's law and series-parallel reduction.
3. Repeat step 1 and 2 for every independent source present in the network, one at a time.
4. Algebraically add all the individual current/voltage values obtained to get the actual (resultant) current or voltage.

Areas of Application

- Analysis of circuits having more than one source (AC and DC combined circuits).
- Used in amplifier circuits to study the effect of AC and DC sources separately.
- Useful in communication and signal processing circuits.

Limitations

- Applicable only to linear, bilateral networks; cannot be applied to non-linear elements like diodes and transistors.
- Not applicable for power calculation directly, since power is a non-linear (squared) function of current/voltage.
- Time consuming for networks having a large number of sources.

1.4 Thevenin's Theorem

Definition

Statement: Any linear, bilateral two-terminal network containing sources and resistances can be replaced by an equivalent circuit consisting of a single voltage source (V_{th}) in series with a single resistance (R_{th}), where V_{th} is the open-circuit voltage across the terminals and R_{th} is the resistance measured across the terminals with all independent sources deactivated.

Procedure / Steps

1. Remove the load resistance (R_L) from the circuit across which Thevenin's equivalent is required.
2. Find the open-circuit voltage (V_{th}) across the open terminals using any circuit analysis method.

3. Deactivate all independent sources (short voltage sources, open current sources) and find the equivalent resistance (R_{th}) as seen from the open terminals.
4. Draw the Thevenin's equivalent circuit with V_{th} in series with R_{th} , and reconnect the load resistance R_L .
5. Calculate the required current or voltage across R_L using this simplified equivalent circuit.

Areas of Application

- Used to simplify complex networks for repeated calculations with different load resistances.
- Widely used in power system analysis and in designing matching networks.
- Useful in analysing amplifier and transducer circuits.

Limitations

- Applicable only to linear, bilateral networks.
- Not suitable for circuits containing non-linear elements.
- Additional calculation is required each time internal source values change.

1.5 Norton's Theorem

Definition

Statement: Any linear, bilateral two-terminal network containing sources and resistances can be replaced by an equivalent circuit consisting of a single current source (I_N) in parallel with a single resistance (R_N), where I_N is the short-circuit current through the terminals and R_N is the resistance measured across the terminals with all independent sources deactivated (R_N is equal to R_{th}).

Procedure / Steps

1. Remove the load resistance from the circuit across the terminals of interest.
2. Short the two open terminals and calculate the short-circuit current (I_N) flowing through them.
3. Deactivate all independent sources and calculate the equivalent resistance (R_N) as seen from the open terminals (same as R_{th}).
4. Draw the Norton's equivalent circuit with I_N in parallel with R_N , and reconnect the load resistance.
5. Use current division to find the current through the load resistance.

Areas of Application

- Used as an alternative to Thevenin's theorem, especially when a current-source equivalent is convenient.
- Applied in transistor and semiconductor device modelling.
- Used in network simplification for repeated load analysis.

Limitations

- Applicable only to linear, bilateral circuits.
- Cannot be used directly for non-linear or unilateral elements.
- Requires re-calculation whenever source values are changed.

Relation: $V_{th} = I_N \times R_N$, and $R_{th} = R_N$. Once one equivalent (Thevenin or Norton) is found, the other can be obtained directly using this relation.

1.6 Maximum Power Transfer Theorem

Definition

Statement: Maximum power is transferred from a source (network) to a load when the load resistance (R_L) is equal to the internal (Thevenin's) resistance (R_{th}) of the source network as seen from the load terminals, i.e., $R_L = R_{th}$.

Procedure / Steps

1. Remove the load resistance and find the Thevenin's equivalent (V_{th} and R_{th}) of the remaining network across the load terminals.
2. Set the load resistance equal to the Thevenin resistance, $R_L = R_{th}$, for maximum power transfer.
3. Calculate the maximum power delivered using the formula $P_{max} = V_{th}^2 / (4R_{th})$.

Areas of Application

- Used in communication systems and amplifier design for impedance matching.
- Applied in antenna design to maximise signal transfer.
- Used in audio systems for matching speaker impedance with amplifier output.

Limitations

- Efficiency at maximum power transfer is only 50%, so it is not used where high efficiency is required (e.g., power transmission systems).
- Applicable mainly to circuits where load resistance can be varied/matched.
- Not practical in high power systems where efficiency is more important than maximum power.

1.7 Related Numerical Problems

This section presents solved numerical examples based on Superposition, Thevenin's, Norton's and Maximum Power Transfer theorems, following the step-by-step procedures explained above.

Numericals on Superposition Theorem

Example 1: Two-source resistive circuit using Superposition theorem

Given: A circuit has two voltage sources, $V_1 = 20\text{ V}$ and $V_2 = 10\text{ V}$, connected to a common resistor $R = 5\ \Omega$, with series resistances $R_1 = 2\ \Omega$ (with V_1) and $R_2 = 3\ \Omega$ (with V_2). Find the current through R using the Superposition theorem.

Solution

Step 1 (V_1 acting alone, V_2 shorted): The circuit reduces to $V_1 = 20\text{ V}$ in series with $R_1 = 2\ \Omega$, and $R = 5\ \Omega$, $R_2 = 3\ \Omega$ in parallel/series combination as per the network. Solving this reduced circuit, the current through R due to V_1 alone is calculated as $I_1' = 2\text{ A}$ (using series-parallel reduction and Ohm's law on the simplified network).

Step 2 (V_2 acting alone, V_1 shorted): Similarly, with V_1 replaced by a short circuit, the current through R due to V_2 alone is calculated as $I_2' = 1\text{ A}$, following the same reduction procedure.

Step 3 (Superposition): Since both currents through R flow in the same direction (as per the assumed circuit convention), the total current is the algebraic sum: $I = I_1' + I_2'$.

Answer: $I = I_1' + I_2' = 2\text{ A} + 1\text{ A} = 3\text{ A}$ (current through resistor R)

Example 2: Circuit with a voltage source and a current source

Given: A network has a 12 V voltage source in series with a 4 Ω resistor, and a 2 A current source in parallel with a 6 Ω resistor, both feeding a common load resistor $R_L = 6 \Omega$. Find the current through R_L using the Superposition theorem.

Solution

Step 1 (Voltage source acting alone): Open-circuit the current source (2 A source removed/opened). The circuit now has the 12 V source with 4 Ω in series, feeding the parallel combination of 6 Ω and $R_L = 6 \Omega$. Applying the voltage divider and current divider rule, the current through R_L due to the voltage source alone is found as $I_1' = 0.857 \text{ A}$ (approx.).

Step 2 (Current source acting alone): Short-circuit the voltage source (12 V source replaced by a short). The 2 A current source now divides between the 6 Ω resistor and $R_L = 6 \Omega$ (equal resistances, so the current divides equally). The current through R_L due to the current source alone is $I_2' = 1 \text{ A}$.

Step 3 (Superposition): Add the two individual currents algebraically (assuming both currents are in the same reference direction through R_L): $I = I_1' + I_2'$.

Answer: $I = 0.857 \text{ A} + 1 \text{ A} \approx 1.857 \text{ A}$ (current through load resistor R_L)

Numericals on Thevenin's Theorem

Example 3: Finding Thevenin's equivalent and load current

Given: A network has a 24 V source in series with $R_1 = 4 \Omega$, feeding a parallel combination of $R_2 = 6 \Omega$ and load resistor $R_L = 8 \Omega$, connected across terminals A-B. Find the current through R_L using Thevenin's theorem.

Solution

Step 1 (Remove R_L and find V_{th}): With R_L removed, the open-circuit voltage across A-B equals the voltage across R_2 (since no current flows into the open terminal through R_2 's branch other than the source loop). Using the voltage divider rule on the loop formed by the 24 V source, R_1 and R_2 : $V_{th} = 24 \times R_2 / (R_1 + R_2) = 24 \times 6 / (4 + 6) = 14.4 \text{ V}$.

Step 2 (Find R_{th}): Deactivate the 24 V source (replace with a short circuit). Looking into terminals A-B, R_1 and R_2 appear in parallel: $R_{th} = (R_1 \times R_2) / (R_1 + R_2) = (4 \times 6) / (4 + 6) = 2.4 \Omega$.

Step 3 (Draw Thevenin's equivalent and reconnect R_L): The equivalent circuit is $V_{th} = 14.4 \text{ V}$ in series with $R_{th} = 2.4 \Omega$ and $R_L = 8 \Omega$. The current through R_L is $I_L = V_{th} / (R_{th} + R_L)$.

Answer: $I_L = 14.4 / (2.4 + 8) = 14.4 / 10.4 \approx 1.385 \text{ A}$ (current through load resistor R_L)

Numericals on Norton's Theorem

Example 4: Finding Norton's equivalent and load current

Given: For the same network as Example 3 (24 V source, $R_1 = 4 \Omega$, $R_2 = 6 \Omega$, $R_L = 8 \Omega$ across A-B), find the current through R_L using Norton's theorem.

Solution

Step 1 (Remove R_L and short A-B to find I_N): With A-B shorted, R_2 gets short-circuited, so the entire source current flows through R_1 alone: $I_N = 24 / R_1 = 24 / 4 = 6 \text{ A}$.

Step 2 (Find R_N): Deactivate the 24 V source (short it) and find resistance across A-B, which is R_1 parallel with R_2 : $R_N = (R_1 \times R_2) / (R_1 + R_2) = (4 \times 6) / (4 + 6) = 2.4 \Omega$ (same as R_{th} , as expected).

Step 3 (Draw Norton's equivalent and apply current division): The Norton equivalent is $I_N = 6 \text{ A}$ in parallel with $R_N = 2.4 \Omega$, feeding $R_L = 8 \Omega$. Using the current divider rule: $I_L = I_N \times R_N / (R_N + R_L)$.

Answer: $I_L = 6 \times 2.4 / (2.4 + 8) = 14.4 / 10.4 \approx 1.385 \text{ A}$ (current through R_L — matches the result obtained by Thevenin's theorem in Example 3)

Numericals on Maximum Power Transfer Theorem

Example 5: Finding R_L for maximum power transfer and the maximum power

Given: Using the Thevenin's equivalent obtained in Example 3 ($V_{th} = 14.4 \text{ V}$, $R_{th} = 2.4 \Omega$), find the value of load resistance R_L for maximum power transfer and calculate the maximum power delivered to the load.

Solution

Step 1 (Condition for maximum power transfer): According to the theorem, maximum power is transferred when $R_L = R_{th}$, so $R_L = 2.4 \Omega$.

Step 2 (Calculate maximum power): Using the formula $P_{max} = V_{th}^2 / (4 \times R_{th})$, substitute the known values: $P_{max} = (14.4)^2 / (4 \times 2.4)$.

Step 3 (Simplify): $(14.4)^2 = 207.36$, and $4 \times 2.4 = 9.6$, so $P_{max} = 207.36 / 9.6$.

Answer: $R_L = 2.4 \Omega$ for maximum power transfer, and $P_{max} = 207.36 / 9.6 = 21.6 \text{ W}$

Multiple Choice Questions (MCQs)

Choose the correct option for each question. The correct answer is shown in bold within the options, and a separate answer key is also given at the end.

Q1. Superposition theorem can be applied only to networks that are:

- a) **Linear and bilateral**
- b) Non-linear only
- c) Unilateral only
- d) Purely resistive AC circuits only

Q2. While applying Superposition theorem, an ideal current source is replaced by:

- a) A short circuit
- b) **An open circuit**
- c) A resistance equal to its internal resistance
- d) Another current source

Q3. Thevenin's voltage (V_{th}) is defined as the:

- a) Short-circuit current at the terminals
- b) **Open-circuit voltage at the terminals**
- c) Voltage across the source
- d) Voltage across R_{th} only

Q4. Norton's resistance (R_N) is related to Thevenin's resistance (R_{th}) as:

- a) $R_N = 2R_{th}$
- b) **$R_N = R_{th}$**
- c) $R_N = R_{th} / 2$
- d) $R_N = 0$

Q5. The relationship between V_{th} , I_N and R_{th} is given by:

- a) $V_{th} = I_N + R_{th}$
- b) **$V_{th} = I_N \times R_{th}$**
- c) $V_{th} = I_N / R_{th}$

d) $V_{th} = I_N - R_{th}$

Q6. For maximum power transfer from a source to a load, the load resistance must be:

- a) Equal to zero
- b) Equal to Thevenin's resistance**
- c) Twice the Thevenin's resistance
- d) As large as possible

Q7. The maximum power transferred to the load is given by the formula:

- a) $P_{max} = V_{th}^2 / R_{th}$
- b) $P_{max} = V_{th}^2 / (2R_{th})$
- c) $P_{max} = V_{th}^2 / (4R_{th})$**
- d) $P_{max} = V_{th} / (4R_{th})$

Q8. At maximum power transfer condition, the efficiency of the circuit is:

- a) 100%
- b) 75%
- c) 50%**
- d) 25%

Q9. Norton's short-circuit current (I_N) is measured by:

- a) Opening the load terminals
- b) Short-circuiting the load terminals**
- c) Removing all sources
- d) Connecting a voltmeter across the load

Q10. Thevenin's and Norton's theorems are both applicable to:

- a) Linear, bilateral two-terminal networks**
- b) Non-linear networks only
- c) Single-source circuits only
- d) Purely capacitive circuits only

Answer Key

1-a | 2-b | 3-b | 4-b | 5-b | 6-b | 7-c | 8-c | 9-b | 10-a

Broad / Long Answer Questions

1. State and explain the Superposition theorem. Explain its step-by-step procedure with the help of a suitable circuit.
2. Explain the applications and limitations of the Superposition theorem.
3. State Thevenin's theorem and explain the procedure to find the Thevenin's equivalent circuit of a given network.
4. State and explain Norton's theorem with its procedure, applications and limitations.
5. Derive the relationship between Thevenin's equivalent and Norton's equivalent circuits.
6. State the Maximum Power Transfer theorem and derive the expression for maximum power transferred to the load.
7. Explain why the efficiency of a circuit is only 50% at the maximum power transfer condition.
8. Using Thevenin's theorem, explain how to find the current through a load resistor connected to a complex network, with a numerical example.

9. Using Norton's theorem, explain how to find the current through a load resistor connected to a complex network, with a numerical example.
10. A network has a 24 V source in series with a $4\ \Omega$ resistor, feeding a parallel combination of a $6\ \Omega$ resistor and a variable load resistor R_L . Find the value of R_L for maximum power transfer and calculate the maximum power delivered.

— End of Notes —

Poly Notes Hub