 


Concept of Counter

★ What is a Counter?

- A counter is a **sequential circuit** that goes through a prescribed sequence of states on the application of clock pulses.
- It is used for counting the number of pulses, measuring time intervals, frequency division, sequence generation, etc.



★ Example

A 3-bit counter has 3 flip-flops.

Total states = $2^3 = 8$

Sequence (Up Counter):

Count	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

Then it returns to 0.

★ Basic Operation

- A counter has 'n' flip-flops, so it can have 2^n different states.
- With each clock pulse, it moves from one state to the next state in a sequence.
- After the last state, it returns to the first state and the process repeats.

★ Types of Counters

- Asynchronous (Ripple) Counter**
 - Flip-flops are triggered one after another (ripple effect).
- Synchronous Counter**
 - All flip-flops are triggered simultaneously by the same clock.
- Up Counter**
 - Counts in increasing order (0, 1, 2, 3, ...).
- Down Counter**
 - Counts in decreasing order (... 3, 2, 1, 0).
- Up/Down Counter**
 - Can count in both directions based on a control input.

Difference Between Asynchronous and Synchronous Counter

Feature	Asynchronous (Ripple) Counter	Synchronous Counter
1. Clocking	Only the first flip-flop receives the external clock. Other flip-flops are triggered by the output of the previous flip-flop.	All flip-flops receive the same clock signal simultaneously.
2. Operation	Flip-flops change state one after another, creating a ripple effect .	All flip-flops change state at the same time.
3. Speed	Slower due to cumulative propagation delay in each flip-flop.	Faster since there is no ripple delay.
4. Max. Operating Frequency	Low	High
5. Hardware Complexity	Simple design, requires fewer gates.	More complex , requires additional gates for combinational logic.
6. Power Consumption	Generally lower .	Generally higher .
7. Glitches	More prone to glitches due to propagation delay.	Fewer glitches .
8. Use	Used in simple, low-speed applications like frequency division.	Used in high-speed applications like microprocessors, memory address counters.
9. Example	3-bit Ripple Counter using JK/T flip-flops.	3-bit Synchronous Counter using JK/T flip-flops.

★ Note

Synchronous counters are preferred in modern digital systems due to their high speed and reliability, while asynchronous counters are used in simple and low-cost designs.

Operation of 3-bit Ripple UP/DOWN Counter


with Timing Diagram - Programmable Ripple Counter

Sequential
Logic Circuits

★ Operation of 3-bit Ripple UP/DOWN Counter

- A 3-bit ripple counter uses three flip-flops (FF_0, FF_1, FF_2) to count through $2^3 = 8$ states.
- All flip-flops are JK flip-flops with $J = K = 1$ (toggle mode).
- UP/DOWN control input (U/D):
 $U/D = 1 \rightarrow$ Up counting
 $U/D = 0 \rightarrow$ Down counting
- When $U/D = 1$ (Up), each flip-flop is clocked by the Q output of the previous flip-flop.
- When $U/D = 0$ (Down), each flip-flop is clocked by the $\bar{Q}$ (complement) output of the previous flip-flop.

★ 3-bit Ripple UP/DOWN Counter Circuit

 

★ State Table (Up Count) - U/D = 1

Count (Decimal)	Q_2 (MSB)	Q_1	Q_0 (LSB)
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

Then repeat to 0

★ State Table (Down Count) - U/D = 0

Count (Decimal)	Q_2 (MSB)	Q_1	Q_0 (LSB)
0	0	0	0
7	1	1	1
6	1	1	0
5	1	0	1
4	1	0	0
3	0	1	1
2	0	1	0
1	0	1	1


Then repeat to 0

Features


- Counts in both upward and downward direction.
- Simple design using ripple (asynchronous) configuration.
- Speed is limited by ripple propagation delay.

★ Timing Diagram

(a) UP Count (U/D = 1)

 


(b) DOWN Count (U/D = 0)

 

★ Programmable Ripple Counter

 - A counter can be made programmable to count from any initial value to any final value.
- When the counter reaches the desired final count, it is automatically reset to the initial count.
- This is achieved using combinational decoding and clearing.



Example

To count from 2 (010) to 6 (110) in UP mode

- Load initial count = 2 (010)
- Decode final count = 6 (110) using a 3-input AND gate
- When 110 occurs, $CLR = 0 \rightarrow$ Counter resets to 010

★ Note

Ripple counters are easy to design but slower due to cumulative propagation delay.
 Synchronous counters are preferred in high-speed applications.

Operation of 4-bit Ripple UP/DOWN Counter


with Timing Diagram - Programmable Ripple Counter

Sequential
Logic Circuits

★ Operation of 4-bit Ripple UP/DOWN Counter

- A 4-bit ripple counter uses four JK flip-flops (FF₀, FF₁, FF₂, FF₃) with $J = K = 1$ (toggle mode) to count through $2^4 = 16$ states.
- All flip-flops are triggered on the falling edge of the clock from the previous stage (ripple connection).
- UP/DOWN control input (U/D):
 - $U/D = 1 \rightarrow$ Up counting (use Q output of previous FF)
 - $U/D = 0 \rightarrow$ Down counting (use $\bar{Q}$ output of previous FF)
- When $U/D = 1$ (Up), each flip-flop is clocked by the Q output of the previous flip-flop.
- When $U/D = 0$ (Down), each flip-flop is clocked by the $\bar{Q}$ (complement) output of the previous flip-flop.

★ 4-bit Ripple UP/DOWN Counter Circuit

 

★ State Table (Up Count) - $U/D = 1$

Count (Decimal)	Q ₃ (MSB)	Q ₂	Q ₁	Q ₀ (LSB)
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1

Then repeat to 0.

★ State Table (Down Count) - $U/D = 0$

Count (Decimal)	Q ₃ (MSB)	Q ₂	Q ₁	Q ₀ (LSB)
15	1	1	1	1
14	1	1	1	0
13	1	1	0	1
12	1	1	0	0
11	1	0	1	1
10	1	0	1	0
9	1	0	0	1
8	1	0	0	0


Then repeat to 15.

Features


- Counts in both upward and downward direction.
- Simple ripple (asynchronous) design.
- Uses JK flip-flops in toggle mode.
- Speed is limited by ripple propagation delay.

★ Timing Diagram

(a) UP Count ($U/D = 1$)

 

(b) DOWN Count ($U/D = 0$)

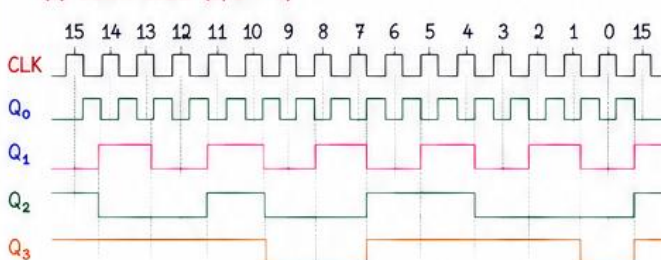


★ Note

Ripple counters are easy to design and require fewer gates, but they are slower due to cumulative propagation delay. Synchronous counters are preferred for high-speed applications.

★ Programmable Ripple Counter

 - A programmable counter can count from any initial value to any final value.
- When the counter reaches the desired final count, it is automatically reset to the initial count.
- This is achieved using combinational decoding and clearing.



Example

To count from 5 (0101) to 13 (1101) in UP mode

- Load initial count = 5 (0101)
- Decode final count = 13 (1101) using a 4-input AND gate
- When 1101 occurs ($Q_3Q_2Q_1Q_0 = 1101$), $CLR = 0 \rightarrow$ Counter resets to 0101
- Counter will repeat the sequence 5, 6, 7, 8, 9, 10, 11, 12, 13, 5


Design of Synchronous Counter with the help of RS Flip-Flop

Sequential Logic Circuits

★ Concept :

- A synchronous counter is a counter in which all flip-flops are triggered by the same clock pulse (common clock).
- Here, RS flip-flops are used to design a synchronous 3-bit binary counter (MOD-8).
- The counter counts in binary sequence from 000 to 111 and then repeats.
- All flip-flops receive the same clock signal, so the state changes simultaneously.

★ Circuit Diagram :

 

★ Truth Table :

Present State ($Q_2 Q_1 Q_0$)	Next State ($Q_2^+ Q_1^+ Q_0^+$)	Input to RS Flip-Flops					
		FF2 ($S_2 R_2$)		FF1 ($S_1 R_1$)		FF0 ($S_0 R_0$)	
0 0 0	0 0 1	0	0	0	0	1	0
0 0 1	0 1 0	0	0	1	0	0	0
0 1 0	0 1 1	0	0	1	0	0	0
0 1 1	1 0 0	1	0	0	1	0	0
1 0 0	1 0 1	0	0	0	0	1	0
1 0 1	1 1 0	0	0	0	0	1	0
1 1 0	1 1 1	0	0	0	0	1	0
1 1 1	0 0 0	0	1	0	1	0	1

Total States = 8 (2^3)


★ Working Principle :

- The counter starts from 000.
- For each clock pulse, the next state is applied to the RS inputs according to the truth table.
- Since all flip-flops get the same clock pulse, the state changes simultaneously.
- The counter goes through 8 states (000 to 111) and then repeats.

Note :

The input combinations for RS flip-flops are based on the state transition table.

★ Output Waveform :

 

★ Key Points :

- Uses RS flip-flops.
- Synchronous counter (common clock).
- Counts in binary sequence (MOD-8).
- All flip-flops receive the same clock pulse.
- Can be extended for more bits (e.g., 4-bit, 5-bit, ...).

★ Summary / Comparison :

Feature	Description
Type	Synchronous counter
Flip-Flop	RS flip-flop
Number of Bits	3 (mod-8)
Clocking	Common clock for all flip-flops
Counting Sequence	000 → 001 → 010 → 011 → 100 → 101 → 110 → 111 → 000


Design of Synchronous Counter with the help of JK Flip-Flop

Sequential
Logic Circuits

★ Concept :

- A synchronous counter is a counter in which all flip-flops are triggered by the same clock pulse (common clock).
- Here, JK flip-flops are used to design a synchronous 3-bit binary counter (MOD-8).
- All flip-flops receive the same clock signal, so the state changes simultaneously.

★ Circuit Diagram :

 

★ Truth Table (General) :


Present State ($Q_2 \ Q_1 \ Q_0$)	Next State ($Q_2^+ \ Q_1^+ \ Q_0^+$)	Input to JK Flip-Flops					
		J_0	K_0	J_1	K_1	J_2	K_2
0 0 0	0 0 1	1	0	1	0	1	0
0 0 1	0 1 0	1	0	1	0	1	0
0 1 0	0 1 1	1	0	1	0	1	0
0 1 1	1 0 0	1	1	0	1	1	0
1 0 0	1 0 1	1	0	1	0	0	1
1 0 1	1 1 0	1	0	1	0	0	1
1 1 0	1 1 1	1	0	0	1	0	1
1 1 1	0 0 0	1	0	0	1	0	1

Total States = $2^3 = 8$

★ Example : 3-bit Synchronous Binary Counter (MOD-8)

Present State ($Q_2 \ Q_1 \ Q_0$)	Next State ($Q_2^+ \ Q_1^+ \ Q_0^+$)
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	1 0 1
1 0 1	1 1 0
1 1 0	1 1 1
1 1 1	0 0 0

★ Output Waveform :

 

★ Key Points :

- Uses JK flip-flops.
- Synchronous counter (common clock).
- $J_0 = K_0 = 1$ (for LSB).
- $J_1 = K_1 = Q_0$.
- $J_2 = K_2 = Q_0 \cdot Q_1$.
- All flip-flops receive the same clock pulse.
- Can be extended for more bits (e.g., 4-bit, 5-bit, ...).

★ Summary / Comparison :

Feature	Description
Type	Synchronous counter
Flip-Flop	JK flip-flop
Number of Bits	3 (mod-8)
Clocking	Common clock for all flip-flops
Counting Sequence	000 → 001 → 010 → 011 → 100 → 101 → 110 → 111 → 000


Design of Synchronous Counter with the help of D Flip-Flop

Sequential
Logic Circuits

★ Concept :

- A synchronous counter is a counter in which all flip-flops are triggered by the same clock pulse (common clock).
- Here, D flip-flops are used to design a synchronous 3-bit binary counter (MOD-8).
- All flip-flops receive the same clock signal, so the state changes simultaneously.

★ Circuit Diagram :

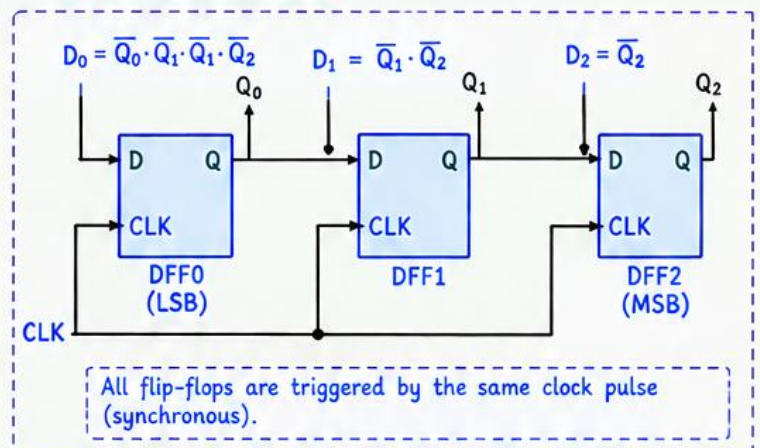

★ Truth Table (General) :

Present State (Q_2 Q_1 Q_0)	Next State (Q_2+ Q_1+ Q_0+)	Input to D Flip-Flops		
		D_2	D_1	D_0
0 0 0	0 0 1	0	0	1
0 0 1	0 1 0	0	1	0
0 1 0	0 1 1	0	1	1
0 1 1	1 0 0	1	0	0
1 0 0	1 0 1	1	0	1
1 0 1	1 1 0	1	1	0
1 1 0	1 1 1	1	1	1
1 1 1	0 0 0	0	0	0

Total States = $2^3 = 8$ (MOD-8)

★ Input Logic for D Flip-Flops :

$$D_0 = \overline{Q_0} \cdot \overline{Q_1} \cdot \overline{Q_2}$$


$$D_1 = \overline{Q_1} \cdot \overline{Q_2}$$

$$D_2 = \overline{Q_2}$$

★ Example (First few states) :

Clock Pulse	Q_2 Q_1 Q_0 (Present)	Q_2 Q_1 Q_0 (Next)
0	0 0 0 →	0 0 1
1	0 0 1 →	0 1 0
2	0 1 0 →	0 1 1
3	0 1 1 →	1 0 0
...	...	...
7	1 1 1 →	0 0 0

★ Output Waveform :

 

★ Key Points :

- Uses D flip-flops.
- Synchronous counter (common clock).
- D_0 , D_1 , D_2 are derived from present state (Q_2 , Q_1 , Q_0).
- All flip-flops receive the same clock pulse.
- Can be extended for more bits (e.g., 4-bit, 5-bit, ...).

★ Summary / Comparison :

Feature	Description
Type	Synchronous counter
Flip-Flop	D flip-flop
Number of Bits	3 (mod-8)
Counting Sequence	000 → 001 → 010 → 011 → 100 → 101 → 110 → 111 → 000
Clocking	Common clock for all flip-flops
Input Logic	$D_0 = \overline{Q_0} \cdot \overline{Q_1} \cdot \overline{Q_2}$, $D_1 = \overline{Q_1} \cdot \overline{Q_2}$, $D_2 = \overline{Q_2}$


Design of Synchronous Counter with the help of T Flip-Flop

Sequential
Logic Circuits

★ Concept :

- A synchronous counter is a counter in which all flip-flops are triggered by the same clock pulse (common clock).
- Here, T flip-flops are used to design a synchronous 3-bit binary counter (MOD-8).
- All flip-flops receive the same clock signal, so the state changes simultaneously.

★ Circuit Diagram :

 

★ Truth Table (General) :

Present State (Q ₂ Q ₁ Q ₀)	Next State (Q ₂₊ Q ₁₊ Q ₀₊)	TInputs		
		(T ₂	T ₁	T ₀)
0 0 0	0 0 1	0	0	1
0 0 1	0 1 0	0	1	1
0 1 0	0 1 1	0	1	1
0 1 1	1 0 0	1	1	1
1 0 0	1 0 1	1	0	1
1 0 1	1 1 0	1	0	1
1 1 0	1 1 1	1	0	1
1 1 1	0 0 0	1	0	1

Total States = $2^3 = 8$ (MOD-8)

★ Input Logic for T Flip-Flops :

For a synchronous counter using T flip-flops :

$$T_0 = 1$$


$$T_1 = Q_0$$

$$T_2 = Q_0 \cdot Q_1$$

★ Example (First few states) :

Clock Pulse	Q ₂ Q ₁ Q ₀ (Present)	Q ₂ Q ₁ Q ₀ (Next)
0	0 0 0 →	0 0 1
1	0 0 1 →	0 1 0
2	0 1 0 →	0 1 1
3	0 1 1 →	1 0 0
...	...	...
7	1 1 1 →	0 0 0

★ Output Waveform :

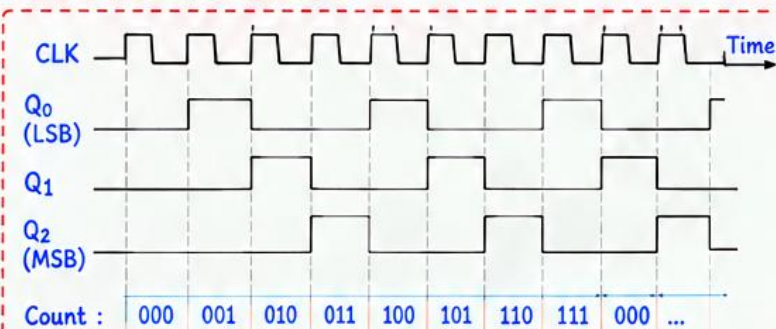

★ Key Points :

- Uses T flip-flops.
- Synchronous counter (common clock).
- $T_0 = 1$, $T_1 = Q_0$, $T_2 = Q_0 \cdot Q_1$.
- All flip-flops receive the same clock pulse.
- Can be extended for more bits (e.g., 4-bit, 5-bit, ...).

★ Summary / Comparison :

Feature	Description
Type	Synchronous counter
Flip-Flop	T flip-flop
Number of Bits	3 (mod-8)
Clocking	Common clock for all flip-flops
Input Logic	$T_0 = 1$, $T_1 = Q_0$, $T_2 = Q_0 \cdot Q_1$


Design of Ring (N:1) Counter

Sequential
Logic Circuits

★ Ring (N:1) Counter

- A Ring counter is a circular shift register in which a single '1' (logic high) circulates through N flip-flops.
- It is a MOD-N counter (has N states).
- It requires N flip-flops and N AND gates (to generate one-hot outputs).
- It is a type of self-starting counter.

 ★ Circuit Diagram of Ring (N:1) Counter (using D Flip-Flops)



The Q output of each flip-flop is connected to the D input of the next flip-flop.
The Q output of the last flip-flop is connected to the D input of the first flip-flop.

★ Operation

- Initially, one flip-flop is preset to 1 and all others are 0.
- On each clock pulse, the single '1' shifts to the next flip-flop in the ring.
- After N clock pulses, the '1' returns to the first flip-flop and the sequence repeats.
- Thus, it has N unique states.

★ Truth Table (General)

Present State						Next State					
Q_{N-1}	Q_{N-2}	...	Q_1	Q_0		Q'_{N-1}	Q'_{N-2}	...	Q'_1	Q'_0	
1	0	0	...	0	0	0	1	0	...	0	0
0	1	0	...	0	0	0	0	1	...	0	0
0	0	1	...	0	0	0	0	0	...	1	0
:	:	:	:	:	:	:	:	:	:	:	:
0	0	0	...	0	1	1	0	0	...	0	0

(Total States = N)

★ Example: 4:1 Ring Counter

State Table


Clock	Count	Q_3	Q_2	Q_1	Q_0
Initial	0	1	0	0	0
1st Pulse	1	0	1	0	0
2nd Pulse	2	0	0	1	0
3rd Pulse	3	0	0	0	1
4th Pulse	4	1	0	0	0

(Sequence repeats after N = 4 states)

★ Outputs

- The counter is decoded so that only the stage holding '1' produces a high output.
- For N flip-flops, N decoded outputs are available.
- At any time, only one output is high (one-hot output).


★ Decoding Logic (For 4:1 Ring Counter)

 

$Y_i = Q_i$ ($i = 0$ to 3)
i.e., Output is HIGH only when the corresponding flip-flop output is 1.

★ Waveform Diagram (4:1 Ring Counter)

 (Assume Initial State: $Q_3 Q_2 Q_1 Q_0 = 1000$)



Key Points

- Ring counter is a MOD-N counter.
- It has N states.
- Only one flip-flop is HIGH at a time.
- It is self-starting.
- Used in sequence generation, timing signals, and control applications.


Johnson Counter (2N:1)

Sequential
Logic Circuits

★ Johnson Counter (2N:1)

- Johnson counter is a modified ring counter.
- In Johnson counter, the inverse ($\bar{Q}$) of the last flip-flop output is fed back to the input of the first flip-flop.
- It uses N flip-flops and has 2N unique states.
- It is a self-starting counter.

 ★ Circuit Diagram of Johnson Counter using N Flip-Flops



The inverse ($\bar{Q}_{N-1}$) of the last flip-flop output is connected to the D input of the first flip-flop.

★ Operation

- Initially, the counter is cleared (all outputs = 0).
- On each clock pulse, bits shift to the right.
- The complement of the last flip-flop output is fed back to the first flip-flop.
- After 2N clock pulses, the sequence repeats.
- It has 2N states.
- Example: For N = 4, total states = 2N = 8.

★ Truth Table (General)

Present State						Next State					
Q_{N-1}	Q_{N-2}	...	Q_2	Q_1	Q_0	Q'_{N-1}	Q'_{N-2}	...	Q'_2	Q'_1	Q'_0
0	0	...	0	0	0	0	0	...	0	0	0
0	0	...	0	0	1	0	0	...	0	0	0
0	0	...	0	1	1	0	0	...	0	0	1
0	0	...	1	1	1	0	0	...	0	1	1
:	:	:	:	:	:	:	:	:	:	:	:
1	1	...	1	1	0	1	1	...	1	0	0
1	1	...	1	0	0	1	1	...	0	0	0


Total States = 2N

★ Example: 4-bit Johnson Counter (N = 4, 2N = 8 states)

Clock Pulse	Q_3	Q_2	Q_1	Q_0
Initial	0	0	0	0
1st	0	0	0	1
2nd	0	0	1	1
3rd	0	1	1	1
4th	1	1	1	0
5th	1	1	0	0
6th	1	0	0	0
7th	0	0	0	0
8th	0	0	0	0 (repeat)

★ Waveform Diagram (Example: 4-bit Johnson Counter)

 Assume Initial State: $Q_3 Q_2 Q_1 Q_0 = 0000$



At any time, either all outputs are 0, or the outputs contain a group of 1's followed by a group of 0's.

★ Key Points

- Johnson counter uses N flip-flops.
- It has 2N states.
- The complement of the last flip-flop output is fed back to the first flip-flop.
- It is self-starting.
- It is widely used in frequency division, sequence generation, and control circuits.

★ Comparison with Ring Counter

Feature	Ring Counter (N:1)	Johnson Counter (2N:1)
Number of States	N	2N
Feedback	Last Q to First D	Complement of Last Q to First D
Self-Starting	No	Yes
State Sequence	One-hot	Twisted Ring (Group of 1's & 0's)

Registers in Digital Electronics

Sequential
Logic Circuits

★ Definition :


A register is a group of flip-flops used to store and temporarily hold binary data.

Since each flip-flop can store 1 bit, an n-bit register requires n flip-flops.

★ Key Points :

- A register is a collection of flip-flops.
- Each flip-flop stores one binary bit (0 or 1).
- Registers are used for data storage and data transfer.
- Data can be shifted left or right in shift registers.
- Registers are important building blocks of digital systems, CPUs, counters and memory circuits.

★ Circuit Diagram (4-bit Register) :

 

★ Example :

A 4-bit register can store 4 binary bits :

1 0 1 1

It uses 4 flip-flops, with each flip-flop storing one bit :




★ Types of Registers :

Common types include :

- ① **SISO** (Serial-In Serial-Out)
- Data enters and exits serially.
- ② **SIPO** (Serial-In Parallel-Out)
- Data enters serially, exits in parallel.
- ③ **PISO** (Parallel-In Serial-Out)
- Data enters in parallel, exits serially.
- ④ **PIPO** (Parallel-In Parallel-Out)
- Data enters and exits in parallel.

★ Types with Diagram :

 

★ Applications :

- Used in data storage and transfer.
- Used in CPUs, microcontrollers and microprocessors.
- Used in counters, shift registers and memory circuits.
- Helps in temporary data holding and synchronization.

★ Summary :

A register is a group of flip-flops that stores binary information.

Register = n flip-flops = n bits.


Serial In Serial Out (SISO) Shift Register Operation with Circuit Diagram

Sequential
Logic Circuits

★ Concept :

- A Serial In Serial Out (SISO) shift register takes input data in serial form and provides output data in serial form.
- It consists of a chain of flip-flops (usually D flip-flops) connected in series.
- With each clock pulse, the data moves from one flip-flop to the next.

★ Circuit Diagram :

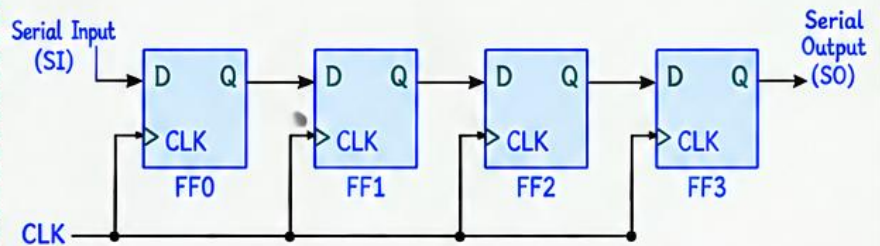

Here, 4 D flip-flops are connected in series. The clock signal is common to all flip-flops.

★ Operation :

- 1 Initially, all flip-flops are cleared ($Q = 0$).
- 2 A serial input bit is applied to the first flip-flop (FF0).
- 3 On each clock pulse, the data moves one stage to the right.
- 4 After 4 clock pulses, the first input bit appears at the output (SO).
- 5 The next bits follow in the same manner.
- 6 Thus, the data is shifted out serially in the same order as it was applied.

★ Truth Table :


Clock Pulse	SI (Input)	Q_0	Q_1	Q_2	Q_3 (SO)
Initial	—	0	0	0	0
1	1	1	0	0	0
2	0	0	1	0	0
3	1	1	0	1	0
4	1	1	1	0	1

(Example: Input sequence = 1 0 1 1)

★ Note :

- The output appears after 4 clock pulses (for 4-bit register).
- The data moves from left to right.
- The output is delayed by the number of flip-flops.

★ Timing Diagram / Waveform :

 

★ Key Points :

- SISO means Serial In Serial Out.
- Consists of n D flip-flops.
- Data moves from left to right with each clock pulse.
- Output is available after n clock pulses.
- Used in serial data transmission, data storage and conversion.

★ Summary :

Feature	Description
Full Form	Serial In Serial Out (SISO) Shift Register
Flip-flops used	n D flip-flops (in series)
Input	Serial input (SI)
Output	Serial output (SO)
Data movement	Left to right (with clock pulses)
Clocking	Common clock for all flip-flops


Serial In Parallel Out (SIPO) Shift Register Operation with Circuit Diagram

Sequential
Logic Circuits

★ Concept :

- A Serial In Parallel Out (SIPO) shift register takes input data in serial form and provides output data in parallel form.
- It consists of a chain of flip-flops (usually D flip-flops) connected in series.
- After n clock pulses, the data appears at all the output lines simultaneously (in parallel).

★ Circuit Diagram :

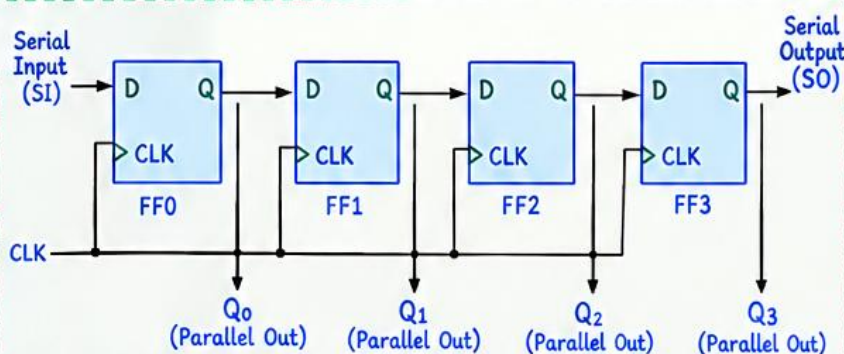

Here, 4 D flip-flops are connected in series.
The Q outputs give parallel data, and the output can also be taken from the last flip-flop for serial output (optional).

★ Operation :


- 1 Initially, all flip-flops are cleared ($Q = 0$).
- 2 A serial input bit is applied to the first flip-flop (FF0).
- 3 On each clock pulse, the data moves one stage to the right.
- 4 After 4 clock pulses (for 4-bit register), the data appears at all the output lines simultaneously, (Q_0, Q_1, Q_2, Q_3).
- 5 The output can also be taken from the last flip-flop as serial output (SO).

★ Truth Table :

Clock Pulse	SI (Input)	Q_0 (FF0)	Q_1 (FF1)	Q_2 (FF2)	Q_3 (FF3)
Initial	-	0	0	0	0
1	1	1	0	0	0
2	0	0	1	0	0
3	1	1	0	1	0
4	1	1	1	0	1

(Example: Input sequence = 1 0 1 1)

★ Timing Diagram / Waveform :

 

★ Key Points :

- SIPO means Serial In Parallel Out.
- S Input is serial, output is parallel.
- Consists of n D flip-flops.
- Data moves from left to right with each clock pulse.
- After n clock pulses, the data is available at all output lines simultaneously.
- Used in data transmission, ADC, DAC, memory systems, and communication systems.

★ Summary :

Feature	Description
Full Form	Serial In Parallel Out (SIPO) Shift Register
Flip-flops used	n D flip-flops (in series)
Input	Serial input (SI)
Output	Parallel output ($Q_0, Q_1, Q_2, \dots, Q_{n-1}$)
Data movement	Left to right (with clock pulses)
Clocking	Common clock for all flip-flops

Parallel In Serial Out (PISO) Shift Register


Operation with Circuit Diagram

Sequential
Logic Circuits

★ Concept :

- A Parallel In Serial Out (PISO) shift register takes input data in parallel form and provides output data in serial form.
- It consists of a chain of flip-flops (usually D flip-flops) with a common clock.
- The data loaded in parallel is shifted out one bit at a time after a control signal is applied.

★ Circuit Diagram :

 

★ Operation :


- 1 Initially, Mode = 0 (Parallel Load).
- 2 On the first clock pulse, the parallel input data (D_3, D_2, D_1, D_0) is loaded into the flip-flops.
- 3 Then, Mode is changed to 1 (Shift).
- 4 With each clock pulse, the data shifts one position to the right.
- 5 The last bit (D_0) appears at the serial output (SO) after 4 clock pulses.

★ Truth Table :

Clock Pulse	Mode	Parallel Input				Serial Output (SO)
		D_3	D_2	D_1	D_0	
Initial	–	Q_3	Q_2	Q_1	Q_0	–
1	0	D_3	D_2	D_1	D_0	–
2	1	–	–	–	–	D_3
3	1	–	–	–	–	D_2
4	1	–	–	–	–	D_1
5	1	–	–	–	–	D_0

(Example: Parallel input = 1 0 1 1 → Serial output = 1 0 1 1)

★ Timing Diagram / Waveform :

 

★ Key Points :

- PISO means Parallel In Serial Out.
- Consists of n D flip-flops.
- Parallel data is loaded when Mode = 0.
- Data shifts right when Mode = 1 (using clock pulses).
- Serial output appears at the last flip-flop (Q_0).
- Widely used in data transmission, ADC, DAC, memory systems and communication systems.

★ Summary :

Feature	Description
Full Form	Parallel In Serial Out (PISO) Shift Register
Flip-flops used	n D flip-flops (in series)
Input	Parallel input (D_3, D_2, D_1, D_0)
Output	Serial output (SO)
Data movement	Right shift (after loading)
Clocking	Common clock for all flip-flops

Parallel In Parallel Out (PIPO) Shift Register


Operation with Circuit Diagram

Sequential
Logic Circuits

★ Concept :

- A Parallel In Parallel Out (PIPO) shift register takes input data in parallel form and provides output data in parallel form.
- It consists of a chain of flip-flops (usually D flip-flops) connected in parallel.
- All flip-flops receive the same clock pulse simultaneously.
- The data is transferred from input to output without shifting.

★ Circuit Diagram :

 

★ Operation :


- 1 Initially, all flip-flops are cleared ($Q = 0$).
- 2 The parallel input data (D_3, D_2, D_1, D_0) is applied to the respective flip-flops.
- 3 On each clock pulse, all flip-flops load the input data simultaneously.
- 4 The same data appears at the output (Q_3, Q_2, Q_1, Q_0).
- 5 The data remains at the output until the next clock pulse with new data.

★ Truth Table :

Clock Pulse	Input (Parallel)				Output (Parallel)			
	D_3	D_2	D_1	D_0	Q_3	Q_2	Q_1	Q_0
Initial	-	-	-	-	0	0	0	0
1	1	0	1	1	1	0	1	1
2	0	1	0	1	0	1	0	1
3	1	1	1	0	1	1	1	0
4	0	0	1	0	0	0	1	0

(Example: Input sequence changes at each clock pulse)

★ Timing Diagram / Waveform :

 

★ Key Points :

- PIPO means Parallel In Parallel Out.
- Consists of n D flip-flops.
- All flip-flops receive the same clock pulse.
- Parallel data is loaded when clock pulse is applied.
- Output is available at the same time as input (no shifting).
- Widely used in data storage, microprocessors, registers and memory systems.

★ Summary :

Feature	Description
Full Form	Parallel In Parallel Out (PIPO) Shift Register
Flip-flops used	n D flip-flops (in parallel)
Input	Parallel input (D_3, D_2, D_1, D_0)
Output	Parallel output (Q_3, Q_2, Q_1, Q_0)
Data movement	No shifting (direct transfer)
Clocking	Common clock for all flip-flops