

FUNDAMENTALS OF ELECTRICAL & ELECTRONICS ENGINEERING

Time Allowed: 1.5 Hours

Full Marks: 60

Answer to Question No.1 is compulsory and Answer any two questions from the rest.

1. Answer the following questions (any twenty): 20x2

- i) Which component opposes any change in current?
 - a) Resistor
 - b) Capacitor
 - c) Inductor
 - d) Diode
- ii) The duration of one cycle known as _____
 - a) waveform
 - b) peak value
 - c) instantaneous value
 - d) period
- iii) In case of ideal current sources, they have _____
 - a) zero internal resistance
 - b) low value of voltage
 - c) large value of current
 - d) infinite internal resistance
- iv) The unit of magnetomotive force is-
 - a) ampere-turn
 - b) weber
 - c) mho
 - d) Maxwell
- v) The property of a material which opposes the creation of magnetic flux is called-
 - a) permeability
 - b) permittivity
 - c) reluctance
 - d) resistance
- vi) The energy stored in a magnetic field is given by (L= self inductance, I= current)-
 - a) $\frac{1}{2}LI^2$
 - b) $\frac{1}{2}IL^2$
 - c) IL^2
 - d) LI^2
- vii) Eddy current loss is directly proportional to (f= frequency , B_m = maximum flux density)-
 - (a) f^2 and B_m^2
 - (b) f and B_m
 - (c) f and B_m^2
 - (d) f^2 and B_m

viii) The direction of induced emf is such that it will oppose the cause to which it is created, is related to _____ law of electromagnetic induction.

- Faraday's
- Lenz's
- Ohm's
- Ampere's

ix) The unit of inductive reactance is--

- Henry
- Farad
- Ohm
- Joule

x) In an ac circuit ' $VI \sin \theta$ ' represents-

- Active power
- Reactive power
- Apparent power
- True power

xi) When sinusoidal voltage is applied across a pure capacitor the current in the capacitor-

- lags applied voltage by 90°
- leads applied voltage by 90°
- is in phase with applied voltage
- is in phase opposition with applied voltage

xii) Peak factor for a sine wave is-

- 1
- 1.414
- 1.11
- 2

xiii) The maximum value of sine wave current is 100 A, the rms value of current in the circuit will be-

- 70.7 A
- 100 A
- 50 A
- 70.7 mA

xiv) Voltage per turn in both primary and secondary winding of a transformer is-

- high in high voltage winding
- low in low voltage winding
- same
- cannot determine

xv) A 10 KVA, 1100/400 V, 50 Hz single phase transformer has 100 turns in the secondary winding. The number of turns in primary winding is _____. (Fill in the blank)

xvi) Direction of rotation of the motor armature/rotor can be determined by applying Fleming's left hand rule .(True/False)

xvii) A diode is a/an-

- bidirectional device
- unidirectional device
- both (a) and (b)
- none of the above

xviii) Free electrons in p type material -

- are majority carrier
- are minority carriers
- both (a) and (b)
- none of the above

xxix) At absolute temperature an intrinsic semiconductor has-

- few free electrons
- few holes
- many holes and free electrons
- no holes and free electrons

xx) An ideal OP-AMP has the following characteristics- (R_{in} =input resistance, A = open loop gain, R_{out} = output resistance)

- $R_{in}=\infty$, $A=\infty$ and $R_{out}=0$
- $R_{in}=0$, $A=\infty$ and $R_{out}=0$
- $R_{in}=\infty$, $A=0$ and $R_{out}=\infty$
- $R_{in}=0$, $A=\infty$ and $R_{out}=\infty$

xxi) The expression of voltage gain in an inverting amplifier using ideal OP-AMP is (R_f =feedback resistance, R_i = input resistance)-

- $-R_f/R_i$
- R_f/R_i
- $1+R_f/R_i$
- $-(1+R_f/R_i)$

xxii) The expression of voltage gain in a non- inverting amplifier using ideal OP-AMP is (R_f =feedback resistance, R_i = input resistance)-

- $-R_f/R_i$
- R_f/R_i
- $1+R_f/R_i$
- $-(1+R_f/R_i)$

xxiii) Which of these sets of logic gates are known as universal gates?

- XOR, NAND, OR
- OR, NOT, XOR
- NOR, NAND, XNOR
- NOR, NAND


xxiv) A digital circuit that can store only 1 bit information-

- NOR gate
- XOR gate
- Flip flop
- AND gate

xxv) The logical sum of two or more than two logical products is termed as

- OR operation
- POS
- SOP
- NAND operation

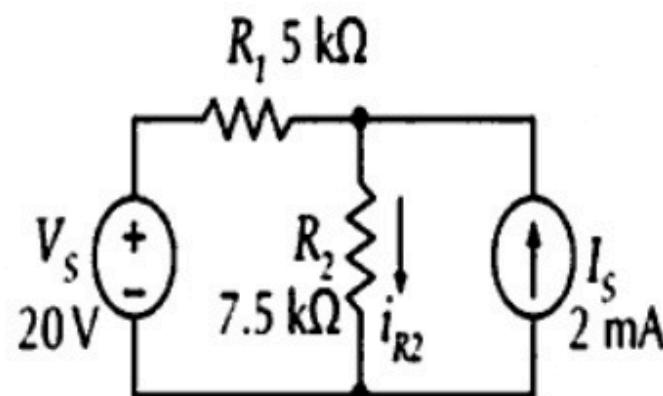2. a) Define periodic & non-Periodic waveform with one example of each.
 b) Using Source transformation principle find out the current through resistance R2.



4+6

3. a) Calculate the RMS and average values of a purely sinusoidal current having peak value 15A.
 b) Draw STAR & DELTA connections. Also write voltage and current relations for both types. 4+6

4. a) Define self & mutual inductance.
 b) State Faradays law of electromagnetic Induction. 5+5

5. a) Define true & reactive power.
 b) Show that in a pure capacitive circuit the current leads the applied voltage by 90 degree. Also show the phasor diagram for the same. 4+6

6. a) Define a Transformer.
 b) A single phase 50Hz transformer has 80 turns on the primary winding & 400 turns on the secondary winding. If the primary winding is connected to a 240 volt, 50 Hz supply, determine the e.m.f induced in the secondary winding. 4+6

7. a) Differentiate between Intrinsic & Extrinsic semiconductor.
 b) Define the term Doping. Give examples of material for creation of p & n-type material. 5+5

8. a) Why is transistor termed as current controlled device?
 b) Explain with diagram the principle of operation of an NPN transistor. 4+6

9. a) Draw the circuit diagram of a non inverting amplifier with feedback using op-amp & derive the expression of gain.
 b) Define Flip-Flop. 7+3

10. Draw the pin diagram of IC 741 OP AMP & describe the function of each pin. 10

11. a) State De Morgan's Theorem.
 b) Draw the NOR gate & write down its truth table. 6+4